
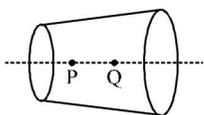


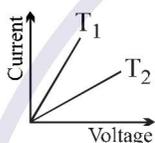1. A wire has a non-uniform cross-section as shown in figure. A steady current flows through it. The drift speed of electrons at points P and Q is v_P and v_Q .




- (1) $v_P = v_Q$ (2) $v_P < v_Q$
 (3) $v_P > v_Q$ (4) Data insufficient
2. The current in a metallic conductor is plotted against voltage at two different temperatures T_1 and T_2 . Which is correct



- (1) $T_1 > T_2$ (2) $T_1 < T_2$
 (3) $T_1 = T_2$ (4) none
3. Two resistances of equal magnitude R and having temperature coefficient α_1 and α_2 respectively are connected in parallel. The temperature coefficient of the parallel combination is, approximately


- (1) $2(\alpha_1 + \alpha_2)$ (2) $\frac{\alpha_1 \alpha_2}{\alpha_1 + \alpha_2}$
 (3) $\frac{\alpha_1 - \alpha_2}{2}$ (4) $\frac{\alpha_1 + \alpha_2}{2}$

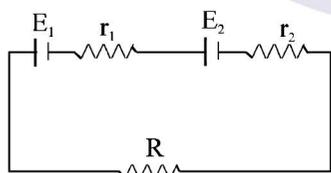4. Under what condition current passing through the resistance R can be increased by short circuiting the battery of emf E_2 . The internal resistances of the two batteries are r_1 and r_2 respectively.




- (1) $E_2 r_1 > E_1 (R + r_2)$
 (2) $E_1 r_2 > E_2 (R + r_1)$
 (3) $E_2 r_2 > E_1 (R + r_2)$
 (4) $E_1 r_1 > E_2 (R + r_1)$

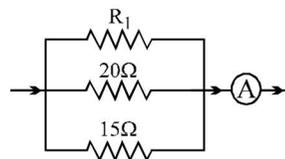
5. In the given circuit the current flowing through the resistance $20\ \Omega$ is 0.3 ampere while the ammeter reads 0.8 ampere. What is the value of R_1 ?



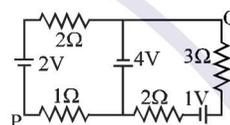
- (1) $30\ \Omega$ (2) $40\ \Omega$
 (3) $50\ \Omega$ (4) $60\ \Omega$
6. In the circuit shown, what is the potential difference V_{PQ} ?



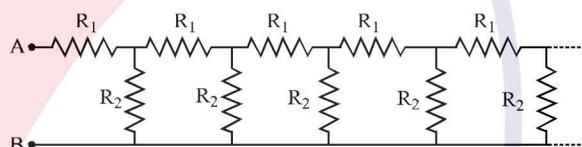
- (1) $+3V$ (2) $+2V$ (3) $-2V$ (4) none
7. Consider an infinite ladder network shown in figure. A voltage V is applied between the points A and B. This applied value of voltage is halved after each section.



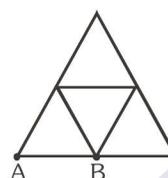- (1) $R_1/R_2 = 1$ (2) $R_1/R_2 = 1/2$
 (3) $R_1/R_2 = 2$ (4) $R_1/R_2 = 3$
8. In the diagram resistance between any two junctions is R . Equivalent resistance across terminals A and B is



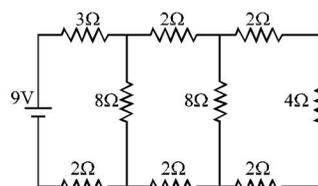- (1) $\frac{11R}{7}$ (2) $\frac{18R}{11}$ (3) $\frac{7R}{11}$ (4) $\frac{11R}{18}$
9. In the circuit shown in the figure, the current through:



- (1) the $3\ \Omega$ resistor is $0.50\ A$
 (2) the $3\ \Omega$ resistor is $0.25\ A$
 (3) $4\ \Omega$ resistor is $0.50\ A$
 (4) the $4\ \Omega$ resistor is $0.25\ A$

CURRENT ELECTRICITY

10. Power generated across a uniform wire connected across a supply is H . If the wire is cut into n equal parts and all the parts are connected in parallel across the same supply, the total power generated in the wire is

(1) $\frac{H}{n^2}$ (2) n^2H (3) nH (4) $\frac{H}{n}$


11. Two bulbs rated (25 W – 220V) and (100W – 220V) are connected in series to a 440 V line. Which one is likely to fuse?

- (1) 25 W bulb (2) 100 W bulb
(3) both bulbs (4) none

12. If the length of the filament of a heater is reduced by 10%, the power of the heater will


- (1) increase by about 9%
(2) increase by about 11%
(3) increase by about 19%
(4) decrease by about 10%

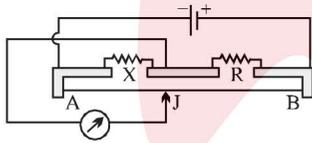13. The figure shows a metre-bridge circuit, with $AB = 100$ cm, $X = 12\Omega$ and $R = 18\Omega$, and the jockey J in the position of balance. If R is now made 8Ω , through what distance will J have to be moved to obtain balance?



- (1) 10 cm (2) 20 cm (3) 30 cm (4) 40 cm

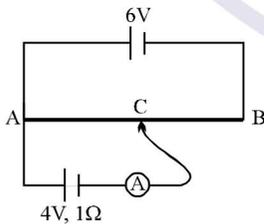14. A 6 V battery of negligible internal resistance is connected across a uniform wire of length 1 m. The positive terminal of another battery of emf 4V and internal resistance 1Ω is joined to the point A as shown in figure. The ammeter shows zero deflection when the jockey touches the wire at the point C. The AC is equal to




- (1) $\frac{2}{3}$ m (2) $\frac{1}{3}$ m (3) $\frac{3}{5}$ m (4) $\frac{1}{2}$ m

15. A potentiometer wire has length 10 m and resistance 10Ω . It is connected to a battery of EMF 11 volt and internal resistance 1Ω , then the potential gradient in the wire is

- (1) 10 V/m (2) 1 V/m (3) 0.1 V/m (4) none

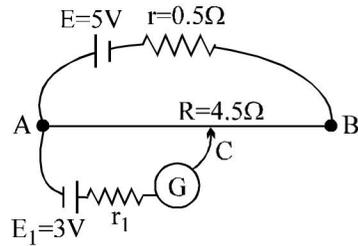
16. In the given potentiometer circuit length of the wire AB is 3 m and resistance is $R = 4.5\Omega$. The length AC for no deflection in galvanometer is



- (1) 2 m (2) 1.8 m
(3) dependent on r_1 (4) none of these

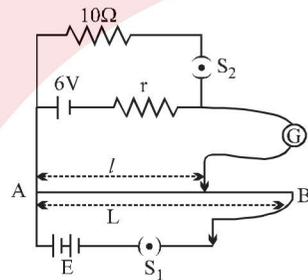
17. In the arrangement shown in figure when the switch S_2 is open, the galvanometer shows no deflection for $l = L/2$. When the switch S_2 is closed, the galvanometer shows no deflection for $l = 5L/12$.

The internal resistance (r) of 6 V cell, and the emf E of the other battery are respectively



- (1) $3\Omega, 8V$ (2) $2\Omega, 12V$
(3) $2\Omega, 24V$ (4) $3\Omega, 12V$

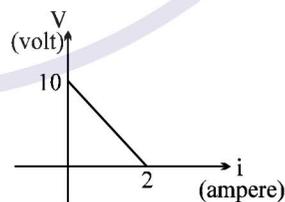18. A battery of emf E and internal resistance r is connected across a resistance R . Resistance R can be adjusted to any value greater than or equal to zero. A graph is plotted between the current (i) passing through the resistance and potential difference (V) across it. Select the correct alternative(s).




- (1) internal resistance of battery is 5Ω
(2) emf of the battery is 20V
(3) maximum current which can be taken from the battery is 4A
(4) $V-i$ graph can never be a straight line as shown in figure.


CURRENT ELECTRICITY

19. In the circuit shown the readings of ammeter and voltmeter are 4A and 20V respectively. The meters are non ideal, then R is :

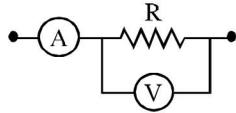- (1) 5Ω
- (2) less than 5Ω
- (3) greater than 5Ω
- (4) between 4Ω & 5Ω




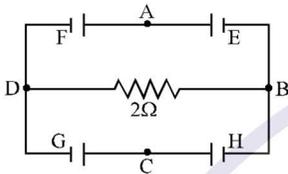20. In the circuit shown E, F, G and H are cells of e.m.f. 2V, 1V, 3V and 1V respectively and their internal resistances are 2Ω , 1Ω , 3Ω and 1Ω respectively.



- (1) $V_D - V_B = -2/13$ V
- (2) $V_D - V_B = 2/13$ V
- (3) $V_G = 21/13$ V = potential difference across G.
- (4) $V_H = 19/13$ V = potential difference across H.

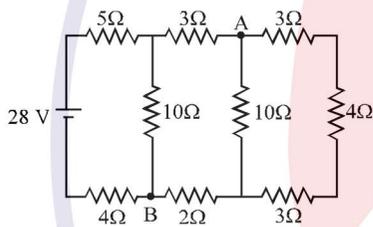21. Consider the circuit shown in the figure



- (1) the current in the 5Ω resistor is 2 A
- (2) the current in the 5Ω resistor is 1 A
- (3) the potential difference $V_A - V_B$ is 10 V
- (4) the potential difference $V_A - V_B$ is 5 V


22. Two bulbs one of 200 volts, 60 watts & the other of 200 volts, 100 watts are connected in series to a 200 volt supply. The power consumed will be

- (1) 37.5 watt
- (2) 160 watt
- (3) 62.5 watt
- (4) 110 watt

23. The length of a potentiometer wire is ℓ . A cell of emf E is balanced at a length $\ell/3$ from the positive end of the wire. If the length of the wire is increased by $\ell/2$. At what distance will the same cell give a balance point.

- (1) $\frac{2\ell}{3}$
- (2) $\frac{\ell}{2}$
- (3) $\frac{\ell}{6}$
- (4) $\frac{4\ell}{3}$

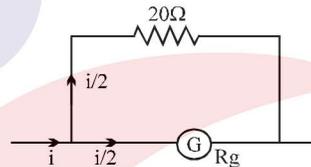24. In a galvanometer, the deflection becomes one half when the galvanometer is shunted by a 20Ω resistor. The galvanometer resistance is



- (1) 5Ω
- (2) 10Ω
- (3) 40Ω
- (4) 20Ω

25. A galvanometer has a resistance of 20Ω and reads full-scale when 0.2 V is applied across it. To convert it into a 10 A ammeter, the galvanometer coil should have a

- (1) 0.01Ω resistor connected across it
- (2) 0.02Ω resistor connected across it
- (3) 200Ω resistor connected in series with it
- (4) 2000Ω resistor connected in series with it

ANSWER KEY

Exercise-1

Que.	1	2	3	4	5	6	7	8	9	10
Ans.	3	2	4	2	4	2	2	4	4	2
Que.	11	12	13	14	15	16	17	18	19	20
Ans.	1	2	2	1	2	4	2	1	3	1,3,4
Que.	21	22	23	24	25					
Ans.	1	1	2	4	2					